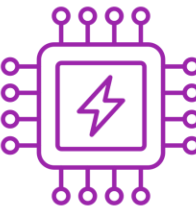


Laboratorio 2:

Bases de Electronica




Agenda

- Motivación
- Herramientas de Simulación en Línea
- Circuitos
 - Circuitos en Serie y en Paralelo: Corriente, Voltaje y Resistencia
 - Ley de Ohm
 - Divisor de Voltaje
 - LEDs



Motivación

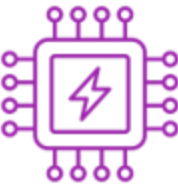- Conocimientos básicos de electrónica son necesarios para seleccionar y utilizar sensores o actuadores en proyectos básicos de IoT.
- Interpretar las señales de voltaje/corriente provenientes de sensores y convertirlas a la magnitud física o química para la cual están diseñados.
- Saber cómo leer fichas de datos (datasheets) de componentes electrónicos.



Herramientas de Simulación en línea


- **DCANLAB:** <https://dcacalab.com/es/lab> (Lab 2)
- **Wowki:** <https://wokwi.com/> (Lab 3 y 4)

- **Otras herramientas:**



CircuitLab: permite diseñar, simular y compartir circuitos.
www.circuitlab.com.


Tinkercad: simulación de circuitos, 3D y programación.
www.tinkercad.com/circuits.

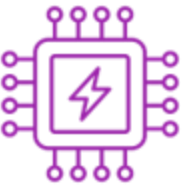Falstad Circuit Simulator: permite diseñar, simular y compartir circuitos. www.falstad.com/circuit/






Circuitos en Serie y Paralelo

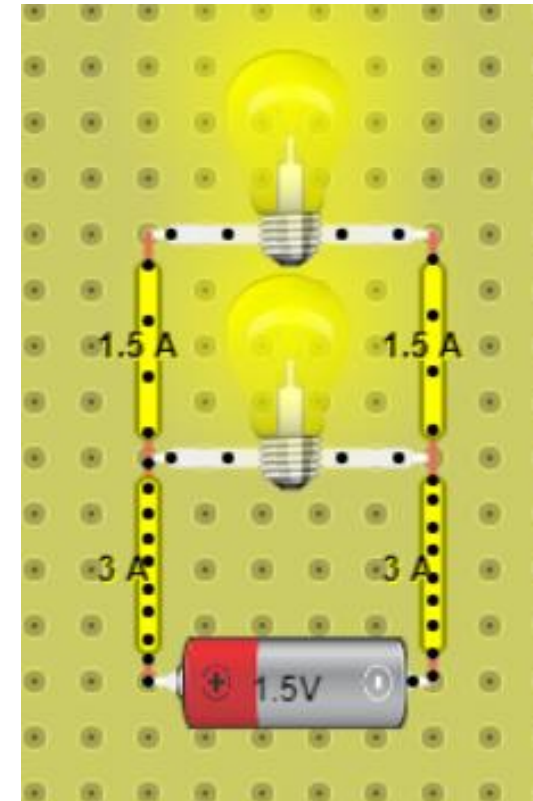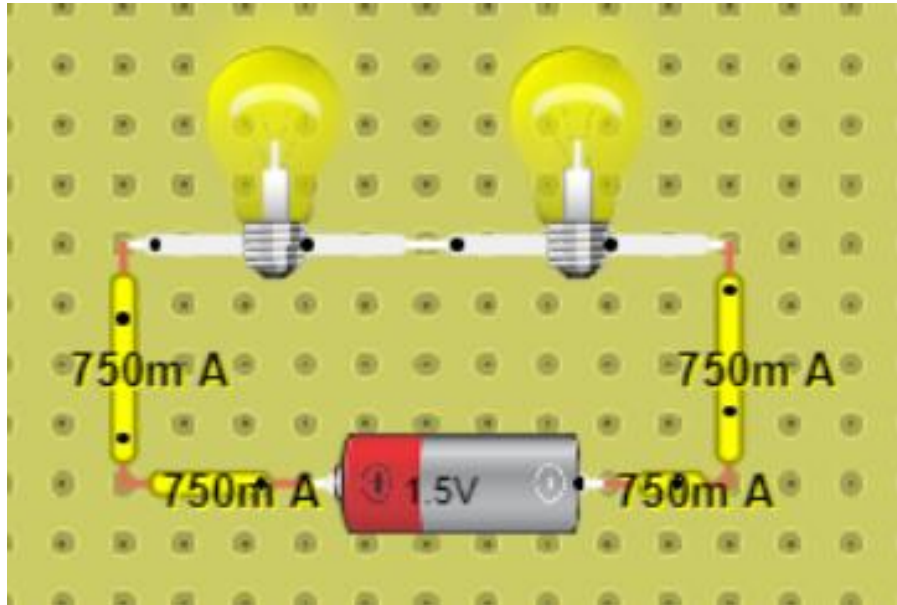


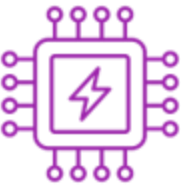



Circuitos en Serie y Paralelo: Corriente

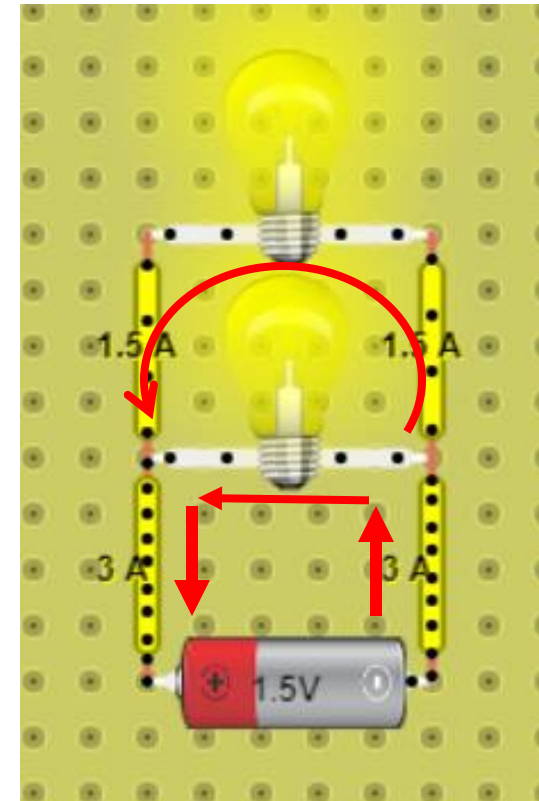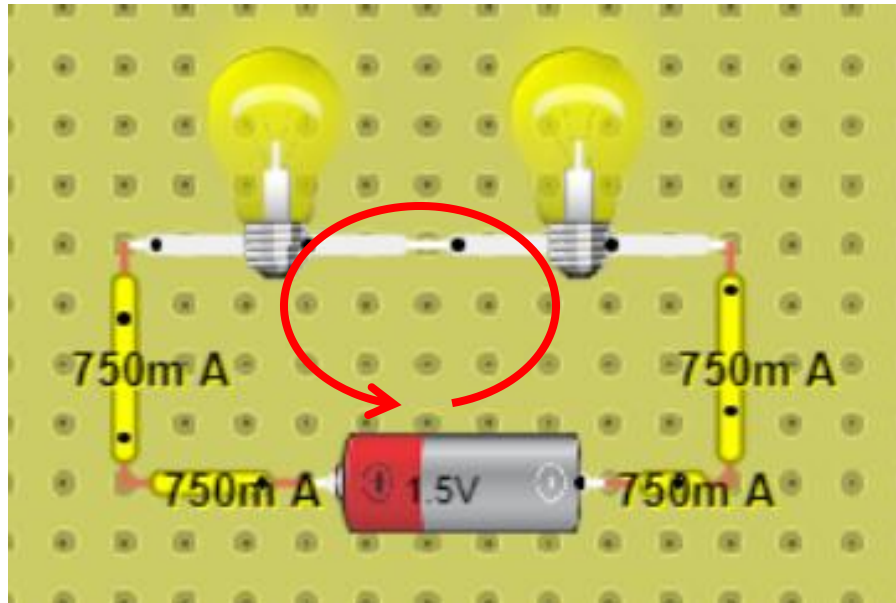

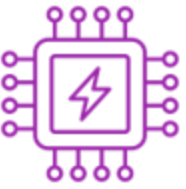

Circuitos en Serie y Paralelo: Voltaje

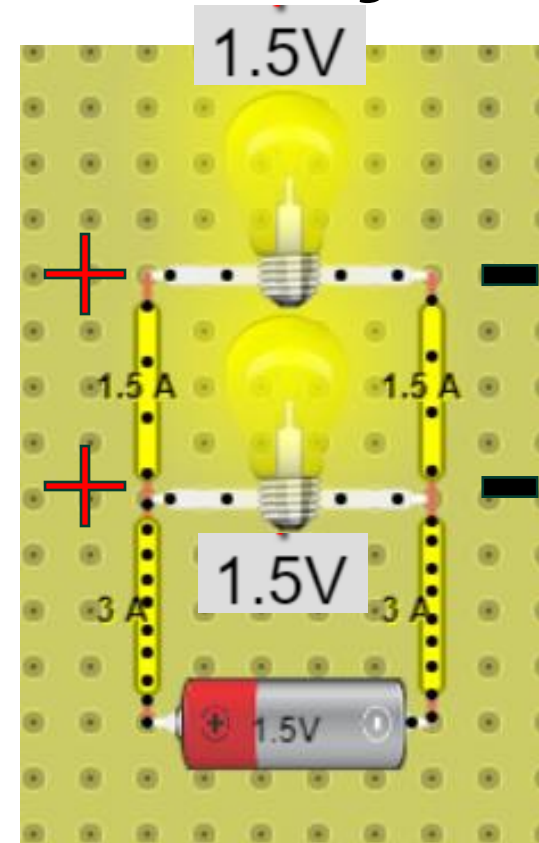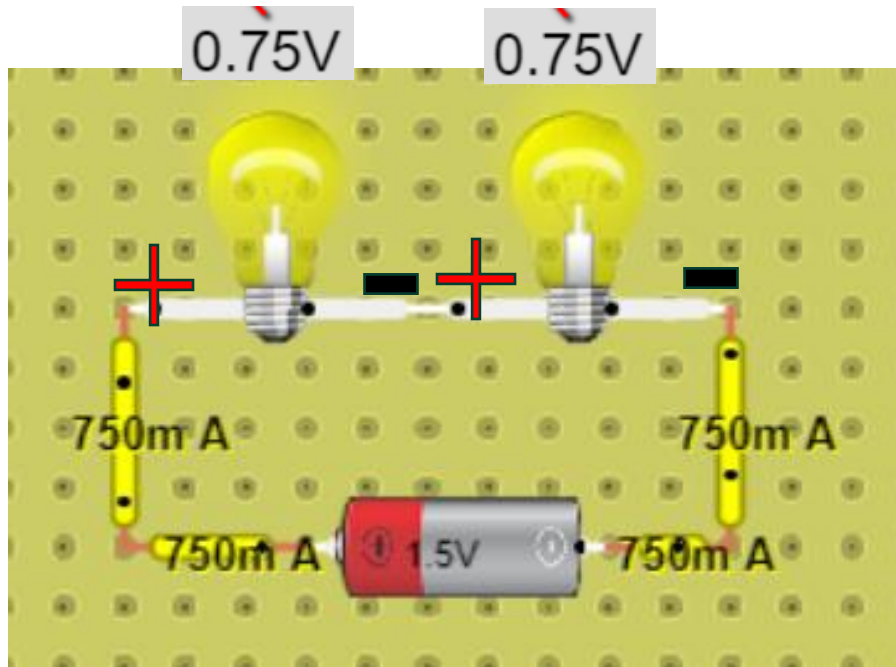

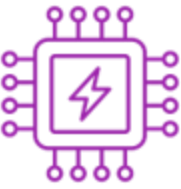

Sumar Resistencias en Series y Paralelo

- $R_{\text{circuito series}} = \frac{V}{I} = \frac{1.5 V}{0.75 A} = 2 \Omega$

$$R_{\text{Total}} = R_1 + R_2, \text{ si } R_1 = R_2 \text{ entonces } ; R_1 = R_2 = 1 \Omega$$

- $R_{\text{circuito paralelo}} = \frac{V}{I} = \frac{1.5 V}{3 A} = 0.5 \Omega$

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2}, \text{ si } R_1 = R_2 \text{ entonces } \frac{1}{0.5 \Omega} = \frac{2}{R_1}; R_1 = R_2 = 1 \Omega$$



Cómo leer Resistencias

- Herramientas online permiten calcular los valores de resistencias:
<https://www.digikey.com/es/resources/conversion-calculators/conversion-calculator-resistor-color-code> .




Diagram illustrating the 4-Band-Code resistor (top) and the 5-Band-Code resistor (bottom).

4-Band-Code Resistor: Shows a resistor with four bands. The tolerance is indicated as 2%, 5%, or 10%. The example value is 560k Ω \pm 5%.

COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)

5-Band-Code Resistor: Shows a resistor with five bands. The tolerance is indicated as 0.1%, 0.25%, 0.5%, or 1%. The example value is 237 Ω \pm 1%.

Resistencia Ajustable

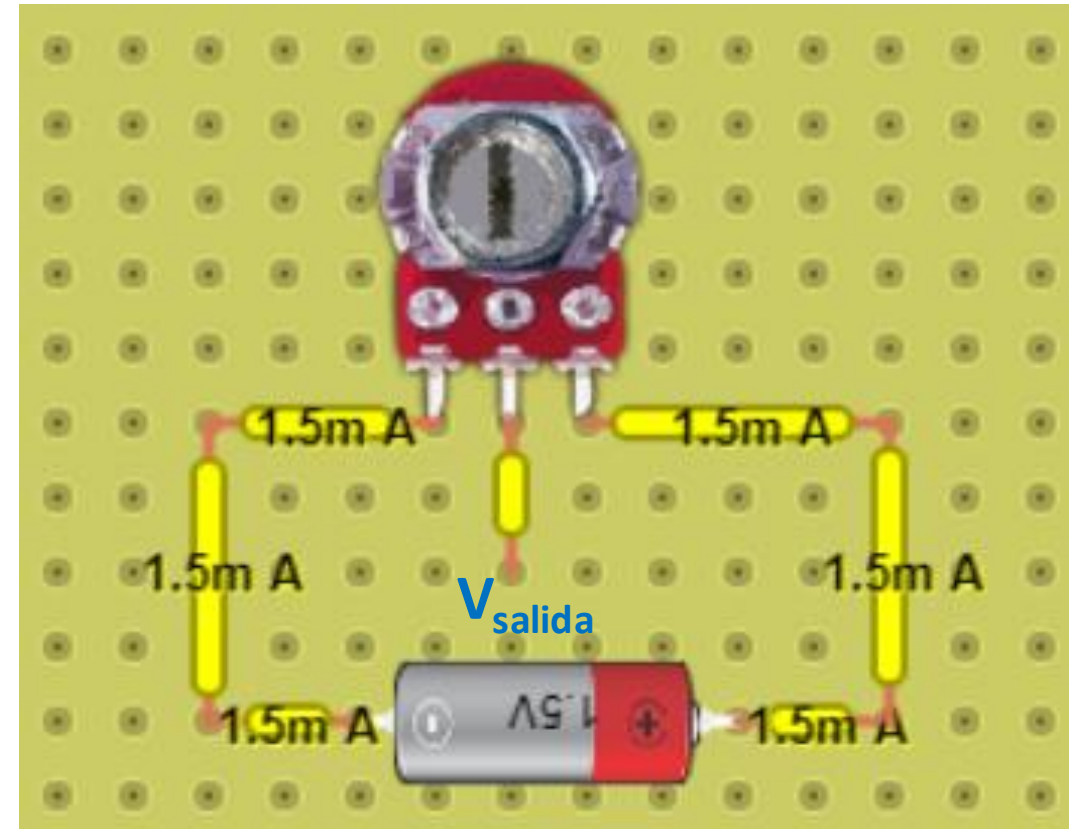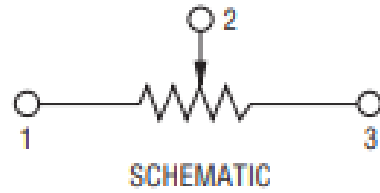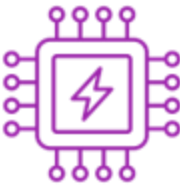



Ley De Ohm

$$V = I \times R$$

$$I = \frac{V}{R}$$


$$R = \frac{V}{I}$$

$$R_{\text{circuito series}} = \frac{V}{I} = \frac{1.5 \text{ V}}{0.75 \text{ A}} = 2 \Omega$$

$$R_{\text{circuito paralelo}} = \frac{V}{I} = \frac{1.5 \text{ V}}{3 \text{ A}} = 0.5 \Omega$$




Divisor de Voltaje

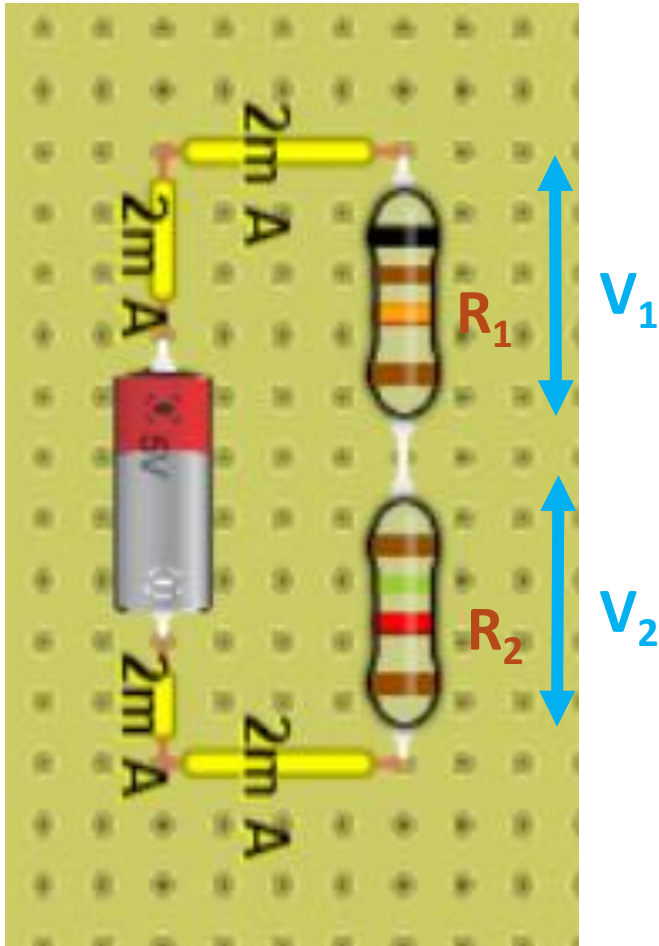


$$V_1 = \frac{R_1 \times V_{Total}}{R_1 + R_2} = \frac{1000\Omega \times 5V}{1000\Omega + 1500\Omega} = 2V$$
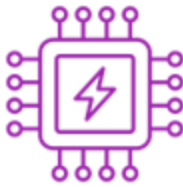
$$V_2 = \frac{R_2 \times V_{Total}}{R_1 + R_2} = \frac{1500\Omega \times 5V}{1000\Omega + 1500\Omega} = 3V$$



Cómo leer señales de voltaje

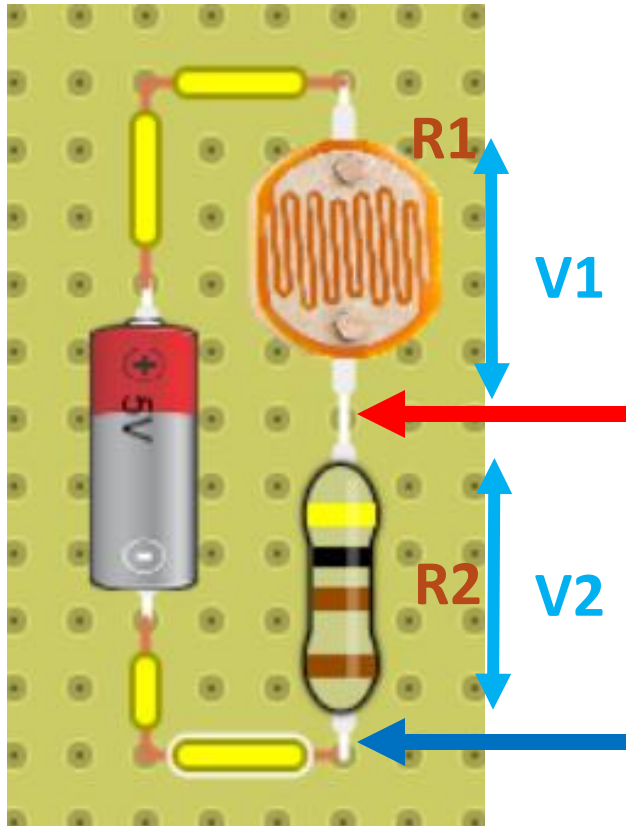

$$V_2 \text{ con emisión de luz} = \frac{R_2 \times V_{Total}}{R_1 + R_2} = \frac{400\Omega \times 5V}{400\Omega + 400\Omega} = 2.5V$$

$$V_2 \text{ sin emisión de luz} = \frac{R_2 \times V_{Total}}{R_1 + R_2} = \frac{400\Omega \times 5V}{1M\Omega + 400\Omega} = 0.0004V$$

Parameter	Conditions	Min.	Typ.	Max.	Units
Cell resistance	1000 lux	-	400	-	Ω
	10 lux	-	9	-	k Ω
Dark resistance	-	1.0	-	-	M Ω
Dark capacitance	-	-	3.5	-	pF
Rise time 1	1000 lux	-	2.8	-	ms
	10 lux	-	18	-	ms
Fall time 2	1000 lux	-	48	-	ms
	10 lux	-	120	-	ms

1. Dark to 110% R_L

2. To $10 \times R_L$



R_L = photocell resistance under given illumination.

Ficha técnica:

https://components101.com/sites/default/files/component_datasheet/LDR%20Datasheet.pdf



Cómo encender un LED

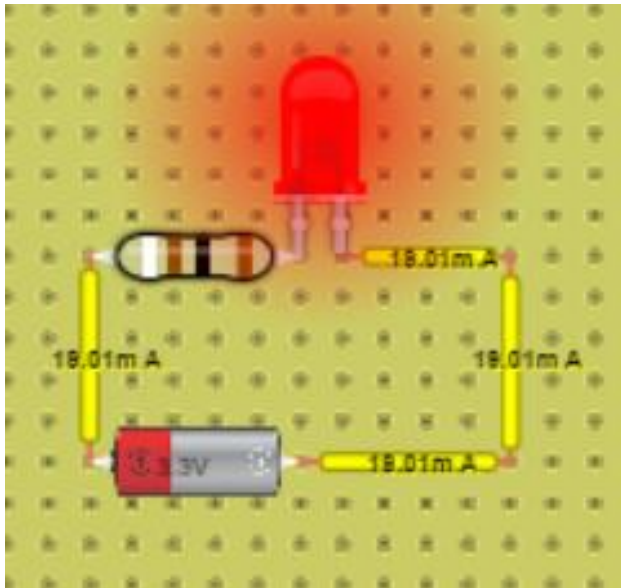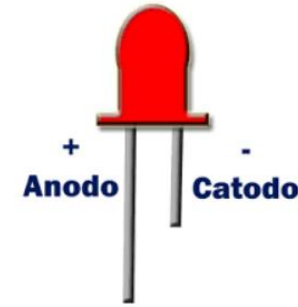

$$R = \frac{V_{total} - V_F}{I_F} = \frac{3.3 V - 1.5V}{20 mA} = 90 \Omega$$

Parameter	Symbol	Test Conditions	Min	Typ	Max	Unit
Luminous Intensity	I_V	$I_F = 20 \text{ mA}$	0.9	3.0	–	mcd
Peak Wavelength	λ_p	$I_F = 20 \text{ mA}$	–	–	660	nm
Spectral Line Half Width	$\Delta\lambda$	$I_F = 20 \text{ mA}$	–	20	–	nm
Forward Voltage	V_F	$I_F = 20 \text{ mA}$	–	1.65	2.0	V
Reverse Current	I_n	$V_R = 5.0V$	–	–	100	λA
Reverse Voltage	λA	$I_R = 100 \lambda A$	–	5.0	–	V
Capacitance	C	$V = 0$	–	35	–	pF
Viewing Angle	$2\theta_{1/2}$	Between 50% Points	–	60	–	degree
Rise Time	t_r	10% – 90% 50 Ω	–	50	–	ns
Fall Time	t_f	90% – 10% 50 Ω	–	50	–	ns

Ficha técnica: <https://us.rs-online.com/m/d/6355b8aba0b01578df0bb7b871ceefd7.pdf>